

**St. Francis Institute of Technology**  
**Class: SE-ITA/ITB Semester: IV A.Y. 2023-2024**  
**Subject: Microprocessor Programming Lab**

**Experiment – 2: Study of Logic Gates**

**1. Aim:** To realize standard and universal logic gates:

- i. To verify the truth tables for basic and universal logic gates.
- ii. To design and implement half adder and full adder circuit.

**2. Prerequisite:** Basic working of logic gates.

**3. Requirements:**

- i. Breadboard, Power supply of 5V, connecting wires, LED, resistor
- ii. ICs – NAND-7400, NOT-7404, EXOR-7486, AND-7408, OR-7432, NOR-7402
- iii. Open source software tool: LogiSim

**4. Pre-Experiment Exercise:**

**A. Basic Gates**

**a. AND Gate:** An AND gate is a multiple input single output gate. For a 2-input AND gate as shown in Fig. 1(a) below, the output Q is true if both the inputs are true.



Fig.1(a). AND Gate

**b. OR Gate:** An OR gate is a multiple input single output gate. For a 2-input OR gate as shown in Fig. 1(b) below, the output Q is true if any one or both the inputs are true.

 


Fig. 1(b). OR Gate

**c. NOT Gate (Inverter):** A NOT gate is a single input single output gate as shown in Fig. 1(c) below. The output Q is inverse of the input A.

 


Fig.1(c). NOT Gate

**B. Universal Gates**

**a. NAND Gate (NAND = Not AND):** This is an AND gate with the output inverted. A NAND gate is a multiple input single output gate. For a 2-input NAND as shown in Fig. 2(a) below, the output Q is true if one or both the inputs are false.



Fig. 2(a). NAND Gate

**b. NOR Gate (NOR = Not OR):** This is an OR gate with the output inverted. A NOR gate is a multiple input single output gate. For a 2-input NOR gate as shown in Fig. 2(b) below, the output Q is true only if both the inputs are false. If any one of the input or both the inputs are true, the output Q is false.

 


Fig. 2(b). NOR Gate

### C. Derived Logic Gates

- a. EX-OR (Exclusive-OR) gate:** This is an OR gate but Excluding the case when both the inputs are true. An EX-OR gate is two input single output gate. For a 2-input EX-OR gate as shown in Fig. 3(a) below, the output Q is true when one of the inputs is true and the other is false i.e. the inputs are DIFFERENT. If both the inputs are false or true, then the output Q is false.

 


Fig. 3(a). EX-OR Gate

- b. EX-NOR (Exclusive-NOR) gate:** This is EX-OR gate with inverted output. An EX-NOR gate is two input single output gate. For a 2-input EX-NOR gate as shown in Fig. 3(b) below, the output Q is true when both the inputs are true or both are false i.e. both the inputs are SAME.

 


Fig. 3(b). EX-NOR Gate

### D. Adder Circuits

- a. Half Adder:** There are two inputs and two outputs in a Half Adder. Inputs are named as A and B, and the outputs are named as Sum (S) and Carry (C). The sum is XOR of the input A and B. Carry is AND of the input A and B. With the help of half adder, one can design a circuit that can perform simple addition with the help of logic gates.
- b. Full Adder:** The full adder is a little more difficult to implement than a half adder. The main difference between a half adder and a full adder is that the full adder has three inputs and two outputs. The two inputs are A and B, and the third input is a carry input CIN. The output carry is designated as COUT, and the normal output is designated as S.

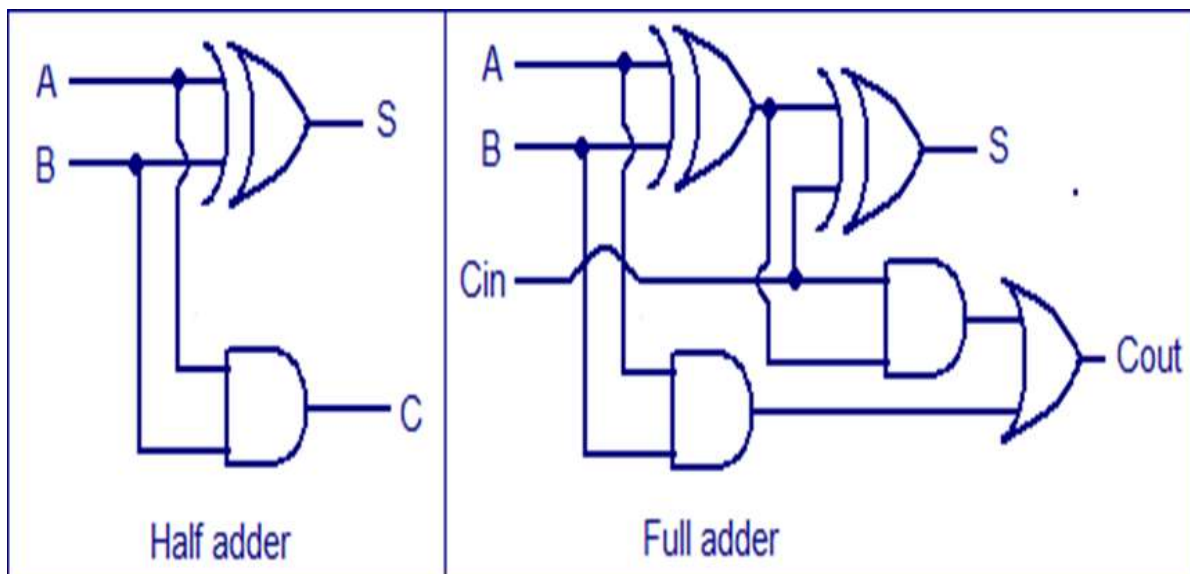


Fig. 4(a). Half Adder

Fig. 4(b). Full Adder

## 5. Laboratory Exercise

### A. Using Hardware

- a. Place the IC on the breadboard. Connect Positive and Negative terminal of Power supply to  $V_{CC}$  and GROUND of the IC.
- b. Use connectors for inputs and connect an LED via a resistor to the output of the IC.
- c. Apply various combinations of inputs according to the truth table and observe the output using LED.

### B. To design and implement half adder and full adder circuit.

- a. Place the gates on the canvas panel of LogiSim. Add the wires and connect it to the gates (input and output).
- b. Add the inputs. Save, Run and Observe the output.

## 6. Post-Experiments Exercise:

### A. Results/Calculations/Observations

- i. Draw the respective truth tables for all the logic gates and universal gates.
- ii. Draw the truth tables for half adder and full adder.

### B. Questions

- i. Why are NAND and NOR gates called as universal gates? Explain with an example for each.
- ii. Realize the following Boolean equation using gates:  $Y = ABC + B\bar{C}D + \bar{A}BC$

### C. Conclusion

Draw conclusion based on the experiment performed. Also mention few applications based on above experiment.


### D. References

Mention two book references and two web references.


## HALF- ADDER

Half Adder take 2 Input A and B and gives two output Sum(S) and Carry(C)

 
1. When A is 0 and B is 0, Sum(S) is 0 and Carry(C) is 0



 
2. When A is 0 and B is 1, Sum(S) is 1 and Carry(C) is 0



 3. When A is 1 and B is 0, Sum(S) is 1 and Carry(C) is 0




 4. When A is 1 and B is 1, Sum(S) is 0 and Carry(C) is 1




## FULL - ADDER

 
1. When A is 0, B is 0 and Cin is 0 , Sum (S) is 0 and Carry out (Cout) is 0



 
2. When A is 0, B is 0 and Cin is 1 , Sum (S) is 1 and Carry out (Cout) is 0.



 
3. When A is 0, B is 1 and Cin is 0 , Sum (S) is 1 and Carry out (Cout) is 0.



 
4. When A is 0, B is 1 and Cin is 1 , Sum (S) is 0 and Carry out (Cout) is 1.



 5. When A is 1, B is 0 and Cin is 0 , Sum (S) is 1 and Carry out (Cout) is 0.




 6. When A is 1, B is 0 and Cin is 1 , Sum (S) is 0 and Carry out (Cout) is 1.





 7. When A is 1, B is 1 and Cin is 0 , Sum (S) is 0 and Carry out (Cout) is 1.



8. When A is 1, B is 1 and Cin is 1 , Sum (S) is 1 and Carry out (Cout) is 1.

